



Roll No:



| | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

BTECH
(SEM II) THEORY EXAMINATION 2021-22
EMERGING DOMAIN IN ELECTRONICS ENGINEERING

Time: 3 Hours**Total Marks: 100****Note:** Attempt all Sections. If you require any missing data, then choose suitably.**SECTION A****1. Attempt all questions in brief.****2*10 = 20**

| Qno | Questions | CO |
|-----|---|----|
| (a) | Discuss the formation of depletion layer in diode. | 1 |
| (b) | Explain the effect of temperature on diode. | 1 |
| (c) | What is difference between BJT and JFET. | 2 |
| (d) | Determine β_{dc} and I_{CBO} , If $I_E = 6mA$, $I_C = 5.92mA$ and $I_{CEO} = 200mA$. | 2 |
| (e) | What do you mean by CMRR in OP-AMP. | 3 |
| (f) | Which is better among microprocessor or microcontroller? Justify your answer with valid reason. | 3 |
| (g) | Determine base of the following: (i) $(345)_{10} = (531)_x$ (ii) $(2374)_{16} = (9076)_x$ | 4 |
| (h) | Write the truth table of two input X-OR gate and two input X-NOR gate. | 4 |
| (i) | Calculate the transmission efficiency if the modulation factor is 0.5. | 5 |
| (j) | Enlist the merits of satellite communication. | 5 |

SECTION B**2. Attempt any three of the following:****10*3 = 30**
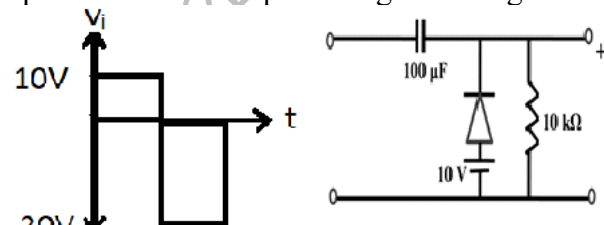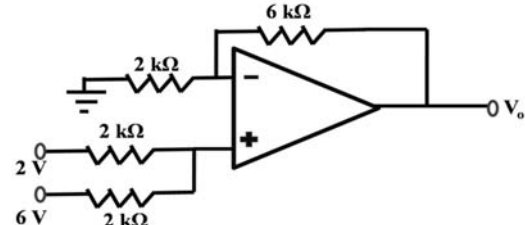
| Qno | Questions | CO |
|-----|---|----|
| (a) | Define Clamper. Determine output voltage for the given network.  | 1 |
| (b) | Draw and explain common base N-P-N Transistor with its input and output characteristic graph. Also write an expression for output current. | 2 |
| (c) | Explain the concept of virtual ground in OP-AMP. Determine output Voltage for given network.  | 3 |
| (d) | Perform following operation as indicated. (i) Determine 2's complement of $(1010.110)_2$. (ii) Convert $(25.125)_{10}$ into Hexadecimal number. (iii) Add binary number $(1011)_2$ and $(1111)_2$. (iv) State De Morgan's Law. (v) Define minterm and maxterm. | 4 |
| (e) | Explain Amplitude modulation. Derive the expression for the total power radiated by the modulated signal. Also calculate modulation efficiency. | 5 |




Roll No:

| | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

BTECH
(SEM II) THEORY EXAMINATION 2021-22
EMERGING DOMAIN IN ELECTRONICS ENGINEERING

SECTION C


3. Attempt any *one* part of the following: 10*1 = 10
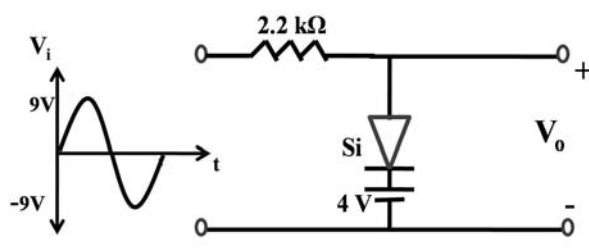
| Qno | Questions | CO |
|-----|--|----|
| (a) | In the bridge rectifier circuit, the secondary voltage $V_s = 100 \sin 50t$ and load resistance is $1k\Omega$. Calculate: (i) DC current (ii) RMS value of current (iii) Efficiency (iv) Ripple factor. | 1 |
| (b) | Determine and draw output voltage for given network.  | 1 |

4. Attempt any *one* part of the following: 10 *1 = 10

| Qno | Questions | CO |
|-----|--|----|
| (a) | Explain the working of enhancement type MOSFET along with their transfer characteristics. | 2 |
| (b) | Describe the construction and working of P-Channel Depletion MOSFET, with characteristic graph. Also Justify that it is a voltage controlled device. | 2 |

5. Attempt any *one* part of the following: 10*1 = 10
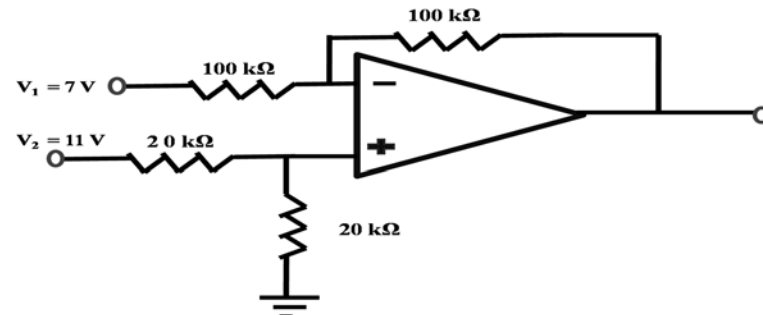
| Qno | Questions | CO |
|-----|---|----|
| (a) | Briefly explain: (i) OP-Amp as Non-Inverting Amplifier. (ii) Inverting summer. (iii) Blue Tooth and Wi-Fi Technology. | 3 |
| (b) | Enlist the characteristics of ideal OP-Amp. Also determine the output voltage of following circuit.  | 3 |



PAPER ID-421107

Printed Page: 3 of 3

Subject Code: KEC201T

Roll No:

| | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

BTECH
(SEM II) THEORY EXAMINATION 2021-22
EMERGING DOMAIN IN ELECTRONICS ENGINEERING

6. Attempt any *one* part of the following: 10*1 = 10

| Qno | Questions | CO |
|-----|---|----|
| (a) | Define universal logic Gates. Realize basic logic gates using NAND and NOR gates. | 4 |
| (b) | Simplify the function $F(A, B, C, D) = \sum m(0, 2, 5, 6, 7, 13, 14, 15) + d(8, 10)$ using K-map and implement the simplified function using NAND gates only. | 4 |

7. Attempt any *one* part of the following: 10*1 = 10

| Qno | Questions | CO |
|-----|---|----|
| (a) | Why do we need modulation? The antenna current of an AM transmitter is 8 A when only the carrier is sent, but it increases to 8.93 A, when the carrier is modulated by a single sine wave. Find percentage modulation. Determine the antenna current when the percent of modulation changes to 0.8. | 5 |
| (b) | An Audio frequency signal $10 \sin 6\pi \times 400t$ is used to amplitude modulate a carrier of $25 \sin 4\pi \times 10^5t$. Calculate (i) Modulation Index (ii) Amplitude of each side band (iii) Total power delivered to the load of $2K\Omega$ (iv) Bandwidth (v) Transmission efficiency | 5 |